

### Ohm's Law



What happens  
when we  
double V?  
→ more and faster  
e<sup>-</sup> movement

Double V → I doubles.


$$\curvearrowright I \propto V$$

Let's look at the units though

$$I \rightarrow \frac{C}{s} \quad V \rightarrow \frac{J}{C} \quad \text{to get}$$

$$V = I X \quad X \text{ must be } \frac{V}{A}$$

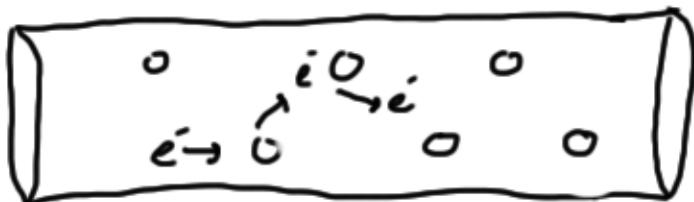? Recognize that the amount of current that can flow per Volt depends on the material.



↗ classical picture to imagine resistance

$$\text{for } V = \underline{I} X$$

This should be large even for small V if the e<sup>-</sup> can travel pretty freely

we call X → R for Resistance

$$V = I R \rightarrow \text{Ohms Law}$$

From above  $R \rightarrow \frac{V}{A}$  ← called "Ohm"


symbol for an Ohm is  $\Omega$  (capital omega)

Wires in most electronics  $\rightarrow$  copper

How much resistance does copper offer?

Depends on how much copper there is

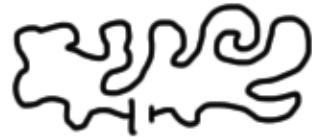Q  $\leftarrow$  has less resistance than  $\rightarrow$



Also depends on cross section.

In general:

$$R = \rho \frac{L}{A}$$


Length of wire  
Area of cross sec.  
 $\rho$   
↳ resistivity

Know R unit is  $\Omega$

What are units of  $\rho$ ?  $\frac{L}{A} \rightarrow \frac{m}{m^2} = \frac{1}{m}$   
so  $\underline{\rho} \rightarrow \underline{\Omega \cdot m}$

Ex.

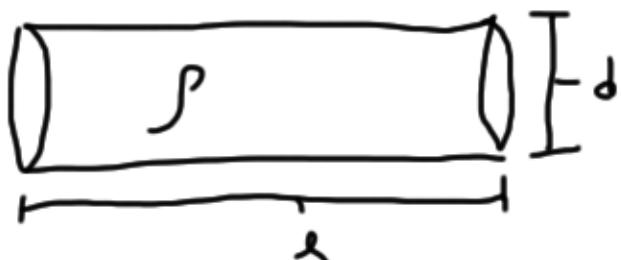Given resistivity of copper what is the resistance of a round wire. You measure the diameter of the wire to be  $d$  and the length to be  $l$



$$R = \rho \frac{L}{A} = \rho \frac{l}{\pi (\frac{d}{2})^2}$$

$$\boxed{R = \rho \frac{l}{\pi d^2}}$$

Ex 2

Building a circuit. Constrained to  $l$  &  $w$  but not  $h$   
using copper (know  $\rho$ ) what is  $h$  such that  $R = R_{\text{want}}$



$$R = \rho \frac{L}{A} \quad R_w = \rho \frac{l}{wh}$$

$$\boxed{h = \frac{\rho l}{w R_w}}$$

Compare some resistances

$$\left. \begin{array}{l} \rho_{\text{copper}} = 1.7 \times 10^{-8} \\ \rho_{\text{gold}} = 2.44 \times 10^{-8} \\ \rho_{\text{rubber}} = 10^{13} - 10^{16} \end{array} \right\} \text{look at wire}$$

10cm long 1mm diam.

$$R_{\text{copper}} = \rho_c \frac{1m}{\pi (1 \times 10^{-3}/2)^2} = \frac{1.7 \times 10^{-8} \times 1m \times 4}{\pi 10^{-6}} = \frac{1.7 \times 10^{-3}}{\pi} \Omega$$

$$R_j = \rho_j \frac{1m}{\pi (1 \times 10^{-3}/2)^2} = [3.1 \times 10^{-3}] \Omega \approx 2 \times 10^{-3} \Omega$$

$$R_r \approx 1 \times 10^{19}$$

Different materials have different  $\rho$ .

How could we change  $\rho$  of the same material.


If the atoms in a material are moving around a lot they will disrupt the movement of electrons.

→ Temperature measures how much the atoms are moving around

However increasing the temp. of a semiconductor increases the conductivity




Very important concept.

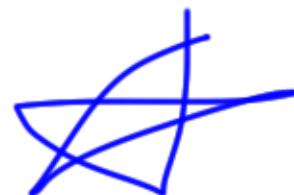

Add energy to a semicond.

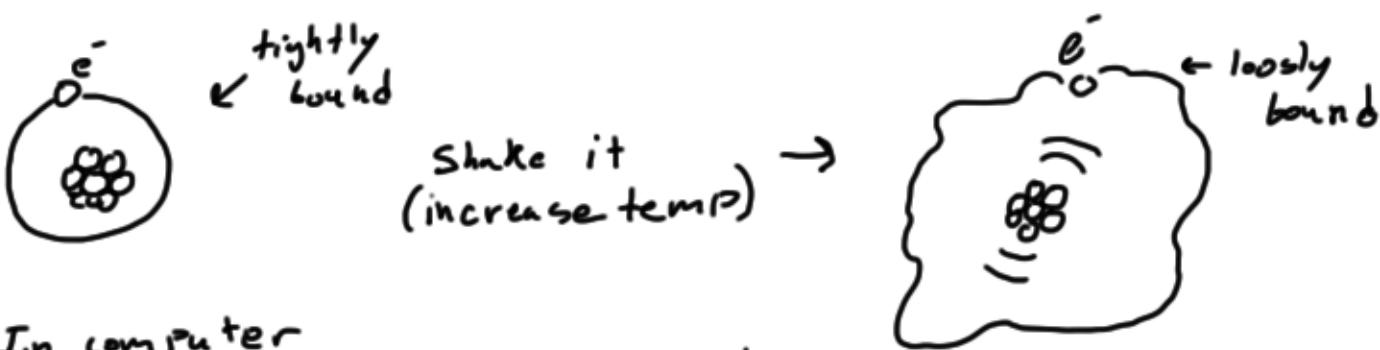electrons can move easily separate from atom → when separate they can move from an applied potential.



In computer switches are made with semicond.s which are off (insulating) normally and can be turned on with an  $\vec{E}$  field that loosens the electrons.

## Power

Current in a circuit transfers energy. When charge moves in a circuit it moves from a high potential to a lower potential.

From 1st physics class we know Power ( $P$ ):

$$P = \frac{\Delta \text{energy}}{\Delta \text{time}} \quad \text{in circuit} \rightarrow P = \frac{\Delta qV}{\Delta t}$$

So 
$$P = IV$$
 units  $\rightarrow W(\text{watt})$


In circuit energy is given to device  
 $\rightarrow$  to conserve energy then energy from battery is lost  $\rightarrow$  does the potential across the battery change? It would but chem. reaction does work to keep potential const.

An electrical component using energy will have a resistance.

$$P = IV \quad V = IR \quad \text{so} \quad P = I(IR) = I^2 R$$

or  $P = \frac{V}{R} V = \frac{V^2}{R}$

## Series resistance

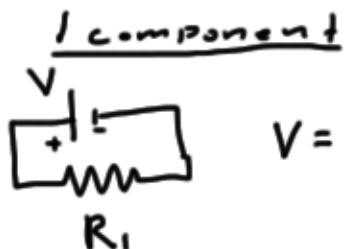


$$V = I R$$

If  $I$  give you  $V & R_1$   
You can find  $I$   
 $I = \frac{V}{R_1}$

Even without  $I$  you can find Power

$$P = \frac{V^2}{R_1} \text{ or with } I \ P = I^2 R_1$$

## 2 components in series

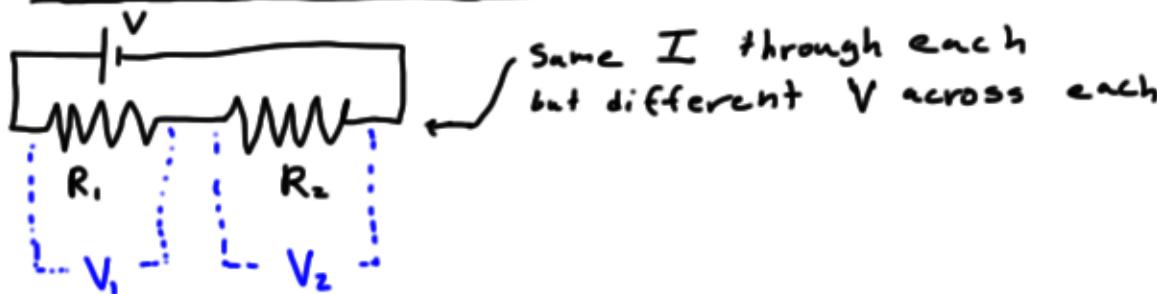


But total pot. across each must add to  
the total  $V$ .

$$\text{so } V = V_1 + V_2 = I R_1 + I R_2 = I (\underbrace{R_1 + R_2}_{R_s}) = I R_s$$

series resistance is  
just the sum of each

$$R_s = \sum_n R_n$$

## 3 components

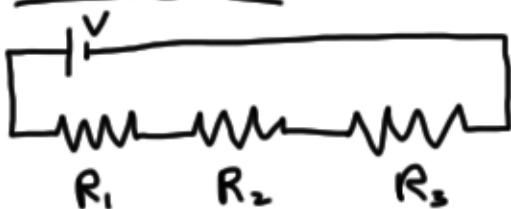

given:  $I, V, R_1, R_2$

find:  $R_s$

$$R_s = R_1 + R_2 + R_3 \quad V = I R_s \quad V = I (R_1 + R_2 + R_3)$$

$$R_3 = \frac{V}{I} - R_1 - R_2$$


Power?

$$P = I^2 R_s = I^2 (R_1 + R_2 + \frac{V}{I} - R_1 - R_2)$$

$$P = IV \leftarrow \text{already knew that!}$$

## Parallel Resistors

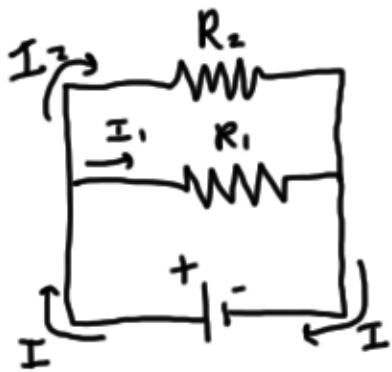- 1) same voltage across components in parallel.
- 2) not necessarily the same current thru



Current must be conserved

$$\text{So } I = I_1 + I_2$$

$$\text{we know } I = \frac{V}{R}$$

$$I = \frac{V_1}{R_1} + \frac{V_2}{R_2} \quad \text{but statement 1)  
tells us } V_1 = V_2$$

$$\text{so } I = V \left( \frac{1}{R_1} + \frac{1}{R_2} \right) \quad V = I \left( \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} \right)$$

$\uparrow \\ R_p$

$$V = IR_p$$

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2}$$

Problems with both series and parallel

**Total  $R = ?$**

Simplify step by step


$R_2$  in parl. with  $R_3$


$$\frac{1}{R_{13}} = \frac{1}{R_2} + \frac{1}{R_3}$$

$R_1$  in series with  $R_{13}$

$$\text{so } R_{123} \text{ or } R_{++} = R_1 + R_{13}$$
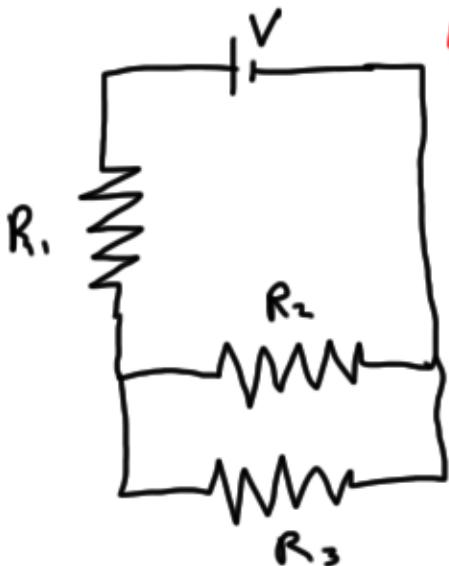
$$R_{++} = R_1 + \frac{1}{\frac{1}{R_2} + \frac{1}{R_3}}$$



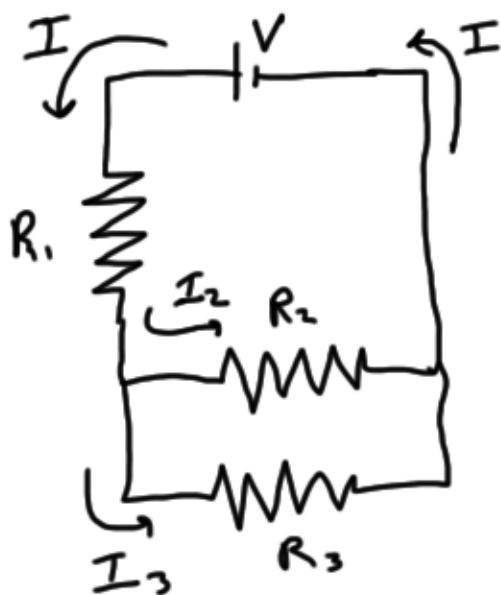

Given:  $V, I, R_1, R_2$

Find:  $R_3$

If we knew  $V_3$  and  $I_3$ ,  
then  $R_3 = \frac{V_3}{I_3}$


- $R_3$  &  $R_2$  in parallel so  $V_3 = V_2$
- $V_1 + V_{23} = V$
- $I = I_2 + I_3$

$$V_3 = V - V_1$$

$$R_3 = \frac{V_3}{I_3} \quad \text{just need } I_3$$

we could write  $I_3 = I - I_2$   
but we would still need  $I_2$

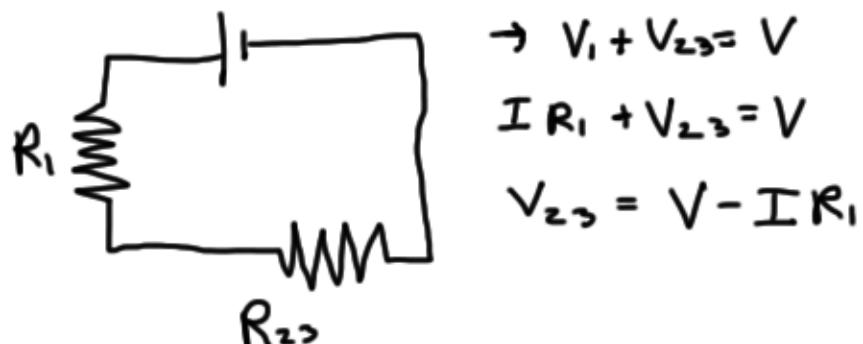→ Next step is to simplify the circuit a little



$$\rightarrow V_1 + V_{23} = V$$

$$IR_1 + V_{23} = V$$

$$V_{23} = V - IR_1$$


$$V_3 = I_3 R_3 \rightarrow V - IR_1 = I_3 R_3$$

$$V_2 = I_2 R_2 \rightarrow V - IR_1 = I_2 R_2$$

$$I_2 = \frac{V - IR_1}{R_2}$$

$$I_3 = I - \frac{V - IR_1}{R_2}$$
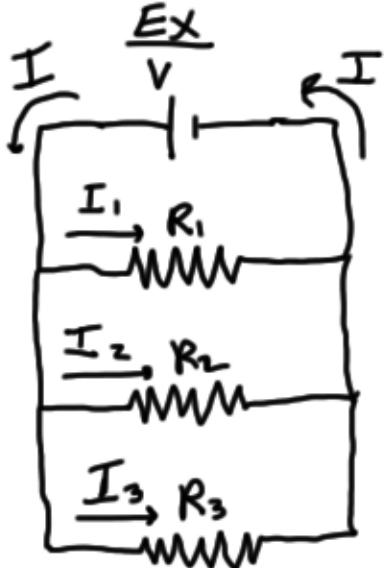
$$R_3 = \frac{V - IR_1}{I - \frac{V - IR_1}{R_2}}$$



Find all I given V, R<sub>1</sub>, R<sub>2</sub>, R<sub>3</sub>

all in parallel so:

$$\frac{1}{R_{\text{tot}}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$V = I R_{\text{tot}} \quad \text{so}$$

$$I = \frac{V}{\left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)}$$

$$I = I_1 + I_2 + I_3$$


$$V_1 = V_2 = V_3$$

$$I_1 = \frac{V_1}{R_1}$$

$$I_3 = \frac{V_3}{R_3}$$

$$I_2 = \frac{V_1}{R_3}$$

$$I_n = \frac{V}{R_n}$$

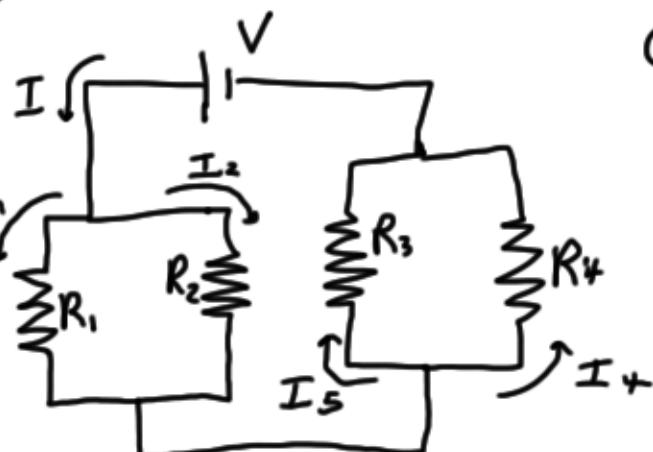

Given  $V, R_1, R_2, R_3, R_4$

find I 4

Start with a relationship  
(eqn.) that contains what  
you know

$$V_4 = I_4 + R_4$$

Start relating things we don't know to things we do know.

$$V_4 = V_3$$

$$I = I_1 + I_2$$

$$V_1 = V_2$$

$$I = I_3 + I_4$$

$$V_{12} + V_{34} = V$$

$$V = I R_{tot}$$

$R_{\text{tot}}$

1st simplify parallel resistors

$$\frac{1}{R_{12}} = \frac{1}{R_1} + \frac{1}{R_2}$$


$$\frac{1}{R_{23}} = \frac{1}{R_2} + \frac{1}{R_3}$$

$$R_{\text{tot}} = R_{12} + R_{23} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} + \frac{1}{\frac{1}{R_2} + \frac{1}{R_3}}$$

$$I = \frac{V}{R_{\text{tot}}}$$



Unsimplify a little

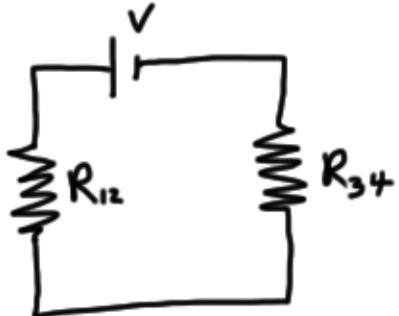

$$V = V_{12} + V_{34}$$

$$V_{34} = V - V_{12}$$

$$V_{34} = V - I R_{12}$$

↑      ↑      ↑  
know   know   know

Back to


$$V_4 = I_4 R_4 \quad V_+ = V_3$$

$$\text{so } I_4 R_4 = V - I R_{12}$$

$$I_4 = \frac{V - I R_{12}}{R_4}$$

← Might include  
full expression  
of  $I$  from above


## Another resistor problem

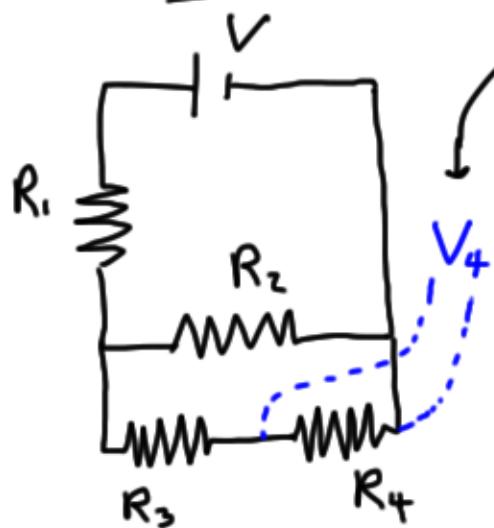

What is  $V_4$ ? i.e. what is the potential across  $R_4$ ?

Given:  $V, R_1, R_2, R_3, R_4$

Draw in your current

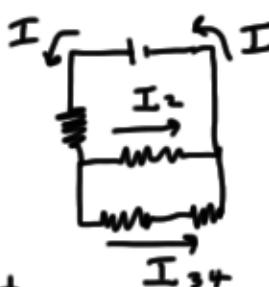


Write an expression that contains what we want to know

$$V_4 = I_{34} R_4$$

Don't know

Simplify circuit.

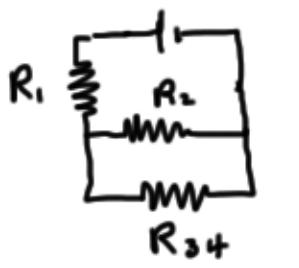


$$V_{34} = V_2$$

$$I = I_2 + I_{34}$$

$$V_3 + V_4 = V_{34}$$

$$\frac{I_{34}}{R_3} + \frac{I_{34}}{R_4} = V_{34} \quad \textcircled{1}$$

Simplify again

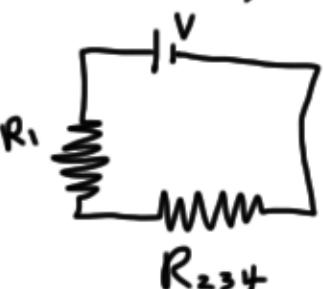

$$V_2 = V_{34} = I R_{234}$$

$$V_2 = I_2 R_2$$

$$I_{34} = I - I_2 = \frac{V}{R_{tot}} - \frac{V_2}{R_2} = \frac{V}{R_{tot}} - \frac{V_{34}}{R_2}$$

$$\textcircled{1} \rightarrow V_{34} = \frac{V}{R+R_3} - \frac{V_{34}}{R_2 R_3} + \frac{V}{R+R_4} - \frac{V_{34}}{R_2 R_4}$$

$$V_{24} + \frac{V_3 +}{R_1 + R_3} + \frac{V_3 +}{R_2 + R_4} = \frac{V}{R_+} \left( \frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$V_{24} \left( 1 + \frac{1}{R_1 + R_3} + \frac{1}{R_2 + R_4} \right) = \frac{V}{R_+} \left( \frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$V_{24} = \frac{V(R_1 + R_3)}{R_1 + R_3 + R_2 + R_4 + R_+}$$

$$\boxed{V_{24} = \frac{V(R_1 + R_3)}{R_1 + R_3 + R_2 + R_4 + R_+}}$$

Skip algeb  
in class.

We have the  
idea


## Kirchoff's Rules

Junction Rule  $\rightarrow$  already been using  
Current in = current out

### loop rule


In a given loop the potential  
drop = Potential gain

### Ex of loop rule

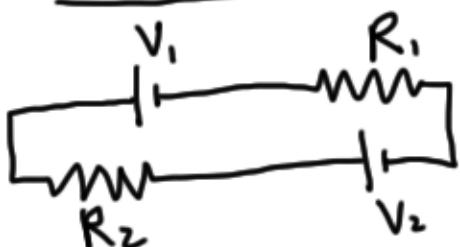

for  $V_2 > V_1$

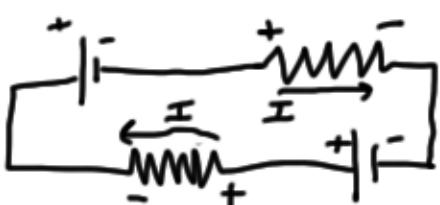If you choose this  
incorrectly it will work out . e  
(get a different sign)




going clockwise a potential  
drop is  $\oplus \rightarrow \ominus$  (Resistor).  
Potential gain  $\ominus \rightarrow \oplus$ .



$$V = IR \text{ so}$$

$$V_1 + IR_1 + IR_2 = V_2$$

drops

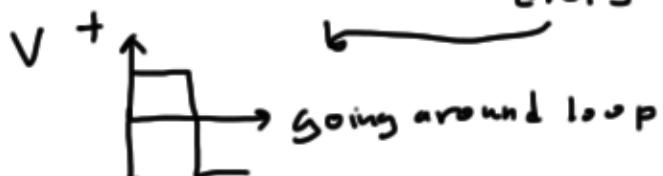


gains

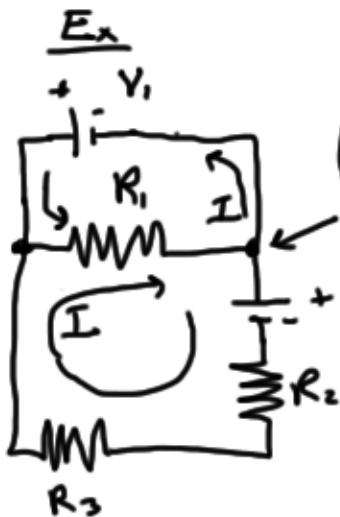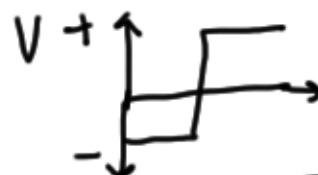

2 junctions


1st Junction rule

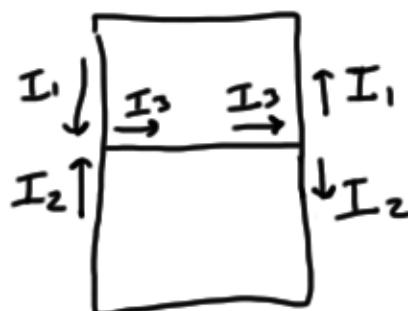re draw current + in and out of junctions



$$\text{so } I_2 + I_1 = I_3$$

Now loop rule

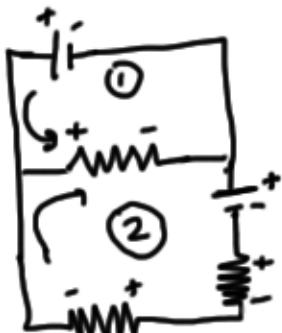

loop ① follow current counterclockwise from upper left corner

$$I_3 R_1 = V_1$$

loop ② clockwise upper left corner

$$I_3 R_1 + V_2 + I_2 R_2 + I_2 R_3 = 0$$

If you were given  $R_1, R_2, R_3, V_1, V_2$   
Could you find all  $I$  ( $I_1, I_2, I_3$ )?

Yes  $\rightarrow$  3 unique equations and 3 unknowns


Batteries can have internal resistance.  
Such a battery could be modeled like



Ex. from book (no #'s here)



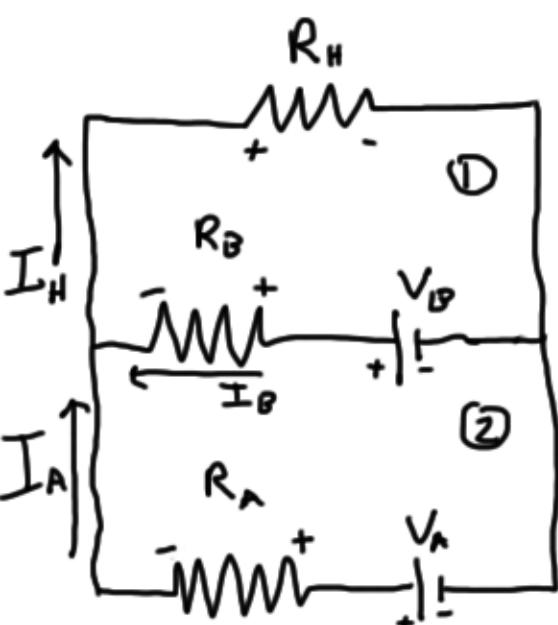Both the battery and alternator have internal resistance  
Circuit:



$$\text{Junction rule: } I_B + I_A = I_H$$

Loop rule:

$$\textcircled{1} \quad \underbrace{I_H R_H + I_B R_B}_{\text{drop}} = \underbrace{V_B}_{\text{gain}}$$

$$\textcircled{2} \quad \underbrace{V_B + I_A R_A}_{\text{drop}} = \underbrace{V_A + I_B R_B}_{\text{gain}}$$

Given  $V_A$ ,  $V_B$ ,  $R_A$ ,  $R_B$ ,  $R_H$  → can find all  $I$   
(3 eqns 3 unknowns)

## Capacitors in Series and Parallel



→ like




If you don't  
change A or d you  
keep the capacitance  
the same

So capacitors in parallel:

$$C_p = C_1 + C_2 + \dots$$

$$q = CV$$

What about in series

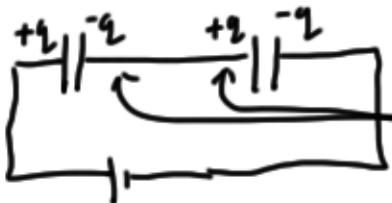

+q & -q cancel →



$$V = V_1 + V_2 = \frac{q}{C_1} + \frac{q}{C_2} = q \left( \frac{1}{C_1} + \frac{1}{C_2} \right) \quad \frac{1}{C_s} = \frac{1}{C_1} + \frac{1}{C_2}$$

$$\frac{1}{C_s} = \frac{1}{C_1} + \frac{1}{C_2} + \dots$$

Opposite to resistors when  $\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \dots$

and  $R_s = R_1 + R_2 + R_3$ .

Using these addition rules &  $q = CV$   
you can solve for various quantities in much the  
same way as the resistor problems.